

$$(1) [k] = \frac{N}{m} = \frac{J}{m^2}, [C] = \frac{C}{\frac{V}{C}} = \frac{C^2}{J}$$

$$[x] = m, [V] = \frac{J}{C}$$

Can increase both  $x$  and  $V$  externally  
decrease

Can't really change  $k$ , could have a "variable capacitor",  
but often practical to build "circuits" of both, with  
different  $k, C$ .

$$(2) C = \frac{Q}{V} \Rightarrow Q = CV = 3.15 \times 10^{-4} \cdot 470 \text{ FV} = 0.148 \text{ [C]}$$

$$(3) U = \frac{CV^2}{2} = \frac{3.15 \times 10^{-4} \cdot 470^2}{2} = 34.8 \text{ J}$$

$$(4) U = \frac{CV^2}{2} = \frac{4.71 \times 10^{-4} \cdot 200^2}{2} = 9.42 \text{ J}$$

Perhaps the decrease is due to:

- Increased safety (lower  $V$ )
- Better\* power production elsewhere in the car \*\* = faster
- Lighter car (less power needed)
- Faster responsiveness (higher  $C$ )

$$(5) C = \epsilon_0 \frac{A}{d} = 8.854 \times 10^{-12} \frac{\text{F}}{\text{m}} \cdot \frac{20}{(100)^2 \text{ m}^2} \cdot \frac{1}{0.002 \text{ m}} = 8.854 \times 10^{-12} \text{ F}$$

(6) It doesn't

$$(7) C \rightarrow 10C = 8.854 \times 10^{-11} \text{ F}$$

(8) More surface area  $\rightarrow$  higher capacitance  $\leftarrow$  wrap spirals  
Easier manufacture / more durable

(9) It will increase! (capacitance goes down, but voltage goes up more)

$$(10) \quad \frac{1}{C} = \frac{1}{2} + \frac{1}{3} \Rightarrow C = \frac{1}{\frac{1}{2} + \frac{1}{3}} = \frac{6}{5}$$


$$(11) \quad C = 3 + 2 = 5$$

$$(12) \quad C = 5 + \frac{6}{5} = \frac{31}{5}$$

$$(13) \quad \frac{1}{C} = \frac{1}{\frac{31}{5}} + \frac{1}{\frac{31}{5}} \Rightarrow C = \frac{1}{\frac{2}{31}} = \frac{31}{2}$$

$$(14) \quad \frac{1}{C} = \frac{1}{10} + \frac{1}{2 \cdot \frac{6}{5}} \Rightarrow C = \frac{1}{\frac{1}{10} + \frac{5}{12}} = \frac{120}{62}$$

(15) Equivalent circuit:

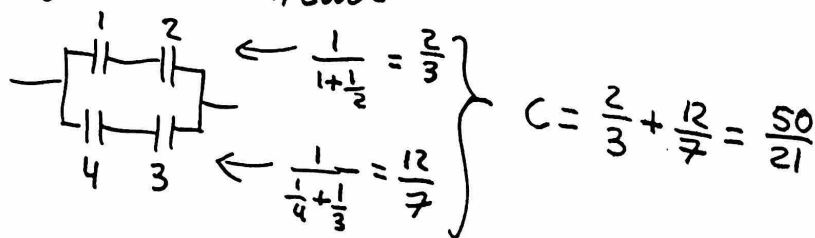

(16) Equivalent Circuit:

