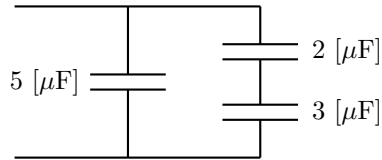



Exercise 12. Circuit II

Calculate the capacitance of the following circuit:




Exercise 13. Circuit III

Calculate the capacitance of the following circuit:

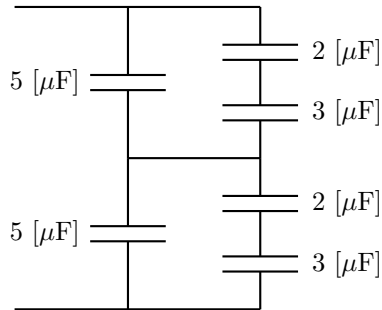


Exercise 14. Circuit IV

Calculate the capacitance of the following circuit:

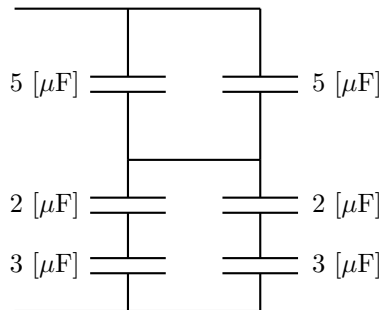

Exercise 15. Circuit V

Calculate the capacitance of the following circuit:

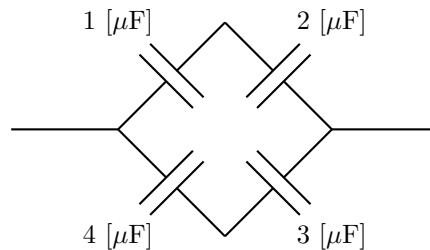

Exercise 16. Circuit VI

Calculate the capacitance of the following circuit:

