

(1) Power is $\left[\frac{J}{s}\right]$

$$IV = \frac{C}{s} \cdot \frac{J}{C} = \left[\frac{J}{s}\right]$$

$$I^2 R = \frac{C^2}{s^2} \cdot \frac{Js}{C^2} = \left[\frac{J}{s}\right]$$

$$\frac{V^2}{R} = \frac{J^2}{C^2} \cdot \frac{1}{\frac{Js}{C}} = \left[\frac{J}{s}\right]$$

(2) $P = IV \Rightarrow 60 = I \cdot 120 \Rightarrow I = 0.5 [A]$

(3) $R = \frac{Pl}{A} = \frac{30 \cdot 0.15}{2 \times 10^{-4}} = 22500 [\Omega]$

(4) $R = \int dR = \int \frac{\rho dx}{A} = \int_0^{0.15} \frac{30x dx}{2 \times 10^{-4}} = 1688 [\Omega]$

(5) current is $\frac{C}{s} \Rightarrow s = \frac{C}{A} \Rightarrow \text{time} = \frac{15}{30000} = 0.0005 [s]$


(6) $P = IV = 30000 \cdot 10\,000\,000 = 300\,000\,000\,000 [W]$ this is big

(7) $P \cdot t = U = qV$
 $P \cdot t = 3 \times 10^{11} \cdot 5 \times 10^{-4} = 1.5 \times 10^8 [J]$
 $q \cdot V = 15 \cdot 10^7 = 1.5 \times 10^8 [J]$


(8) least resistance, also combining electricity (charge) from multiple regions

(9) False. Only the magnitude, but not the direction of ΔV matters. If interested, look up "positive lightning."

(10)

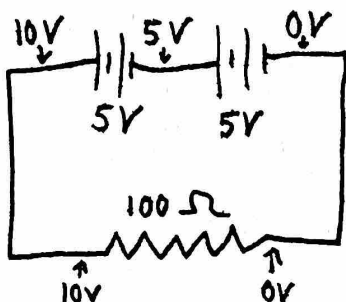

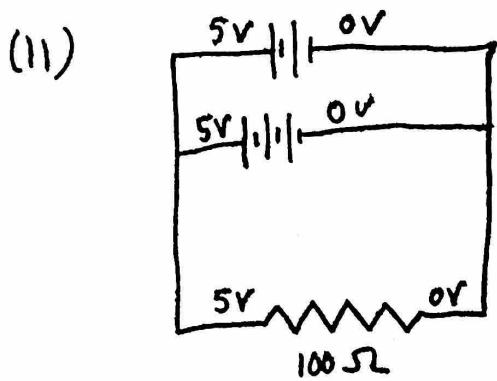$\mathcal{E} = IR \Rightarrow I = \frac{\mathcal{E}}{R} = \frac{10}{100} = 0.1 A$
 everywhere in the circuit



$$\mathcal{E} = IR \Rightarrow I = \frac{\mathcal{E}}{R} = \frac{5}{100} = 0.05 \text{ A}$$

However, if these are the same batteries from (10), they will last longer

(12) $R = 30 + 50 = 80 \Omega$

(13) $\frac{1}{R} = \frac{1}{50} + \frac{1}{30} \Rightarrow R = \frac{1}{\frac{1}{50} + \frac{1}{30}} = 10 \cdot \frac{1}{\frac{3+5}{15}} = \frac{150}{8}$



$35 \Omega \rightarrow$
 $\infty \Omega \leftarrow$



$\frac{1}{R} = \frac{1}{30} + \frac{1}{5} \Rightarrow \frac{30}{7} \Omega \rightarrow$
 $30 \Omega \leftarrow$