

1. (b)
2. (c)
- 3.

$$\begin{aligned}
 P_{\text{rms}} &= \sqrt{\int_T dt P^2(t)/T} \\
 &= \sqrt{\int_T dt (I_0 \cos(\omega t) V_0 \cos(\omega t + \theta))^2/T} \\
 &= I_0 V_0 \sqrt{\int_T dt [\cos(\omega t)(\cos(\omega t) \cos(\theta) - \sin(\omega t) \sin(\theta))]^2/T} \\
 &= I_0 V_0 \sqrt{\int_T dt [[1 - \cos(2\omega t)] \cos(\theta)/2 - \sin(2\omega t) \sin(\theta)/2]^2/T} \\
 &= (I_0 V_0 \cos(\theta)/2) \sqrt{\int_T dt [1 - \cos(2\omega t) - \sin(2\omega t) \tan(\theta)]^2/T} \\
 &= I_0 V_0 \cos(\theta)/2
 \end{aligned}$$

4. (a)
- 5.

$$Z_{\text{circuit}} = \frac{1}{\frac{1}{Z} + \frac{1}{Z}} + Z + \frac{1}{\frac{1}{Z+Z} + \frac{1}{\frac{1}{\frac{1}{Z} + \frac{1}{Z}} + Z}} = \frac{33}{14} Z \quad (1)$$

6. $Z = Z_L + Z_C + Z_R = i\omega L + 1/i\omega C + iR$, now $dZ/d\omega = iL - 1/i\omega^2 C$ so set $L + 1/\omega^2 C = 0$, and find $\omega = 1/\sqrt{LC}$
7. $V_L(t) = I(t)Z_L = I \sin(\omega t)i\omega L$, $V_C(t) = I(t)Z_C = I \sin(\omega t)/i\omega C$, $V_R(t) = I(t)Z_R = I \sin(\omega t)R$, so we see that $\theta(V_L(t)) = \tan^{-1}(I \sin(\omega t)\omega L/0) = \tan^{-1}(\pm\infty) = \pm\pi/2$, likewise $\theta(V_C(t)) = \mp\pi/2$, and $\theta(V_R(t)) = 0$, all independent of the resonant condition.
8. $Z_{\text{circuit}} = R - i/7\omega C$
9. $V_R(t) = I(t)Z_R = \frac{V_0 \sin(\omega t)}{R - i/7\omega C} R = V_0 R \sin(\omega t) \frac{R + i/7\omega C}{R^2 + 1/(7\omega C)^2}$
 $V_{3C} = I_{3C}(t)Z_{3C} = \frac{3}{7} \frac{V_0 \sin(\omega t)}{R - i/7\omega C} \frac{1}{3i\omega C} = \frac{1}{7\omega C} V_0 \sin(\omega t) \frac{1/7\omega C - iR}{R^2 + 1/(7\omega C)^2}$
 Yes, $V_{3C}(t) = V_{4C}(t)$: they are in parallel!
10. $\theta(V_R(t)) = \tan^{-1}(\frac{1}{7R\omega C})$, $\theta(V_{3C}(t)) = \tan^{-1}(-7R\omega C)$
11. $a = R + 1/R((1/R^2) + (\omega C - 1/\omega L)^2)$, $b = \omega L - (\omega C - 1/\omega L)/((1/R^2) + (\omega C - 1/\omega L)^2)$, $\omega_{\text{resonant}} = 0$
12. They are both zero!
13. $R' = R$, $L' = 2L/3$. They are the same because the inductors are in parallel and so cannot have a different phase angle.
14. $\theta(V_L) = \tan^{-1}(3R/2\omega L)$, $\theta(V_R) = \tan^{-1}(-2\omega L/3R)$