

**Exercise 1. Average Voltage**

If the voltage is  $V(t) = V_0 \sin(\omega t)$ , what is the average voltage?

- (a)  $V_{\text{avg}} = 4V_0/\omega$
- (b)  $V_{\text{avg}} = 2V_0/\pi$  \*
- (c)  $V_{\text{avg}} = V_0/\sqrt{2}$
- (d)  $V_{\text{avg}} = 4V_0 \sin(\omega t)/\omega$
- (e)  $V_{\text{avg}} = 2V_0 \sin(\omega t)/\pi$
- (f)  $V_{\text{avg}} = V_0 \sin(\omega t)/\sqrt{2}$

**Exercise 2. RMS Voltage**

If the voltage is  $V(t) = V_0 \sin(\omega t)$ , what is the RMS voltage?

- (a)  $V_{\text{rms}} = 4V_0/\omega$
- (b)  $V_{\text{rms}} = 2V_0/\pi$
- (c)  $V_{\text{rms}} = V_0/\sqrt{2}$  \*
- (d)  $V_{\text{rms}} = 4V_0 \sin(\omega t)/\omega$
- (e)  $V_{\text{rms}} = 2V_0 \sin(\omega t)/\pi$
- (f)  $V_{\text{rms}} = V_0 \sin(\omega t)/\sqrt{2}$

**Exercise 3. RMS Power**

If  $P_{\text{rms}} = \sqrt{\int_T dt P^2(t)/T}$ , and  $P = IV$  where  $I(t) = I_0 \cos(\omega t)$  and  $V = V_0 \cos(\omega t + \theta)$ , show that  $P_{\text{avg}} = I_0 V_0 \cos(\theta)/2$ .  
 Hint:  $\cos(\alpha + \beta) = \cos(\alpha)\cos(\beta) - \sin(\alpha)\sin(\beta)$ .


**Exercise 4. Phase Angle**

Let  $f(t) = (1 - \sin(t)/t) + 2i$ . What is the phase angle for large times?

- (a)  $\theta(f(t)) = \tan^{-1}(2)$  \*
- (b)  $\theta(f(t)) = \tan^{-1}(\pi/2)$
- (c)  $\theta(f(t)) = \tan^{-1}(1/2)$
- (d)  $\theta(f(t)) = \tan^{-1}(2/\pi)$


**Exercise 5. Equivalent Impedance**

Find the equivalent impedance of the following circuit:

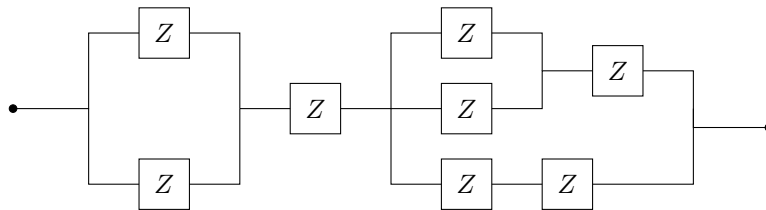

**Exercise 6. Resonance I**


Resonance occurs when impedance is at its minimum. Find  $\omega$  such that the impedance is minimized in the following circuit:

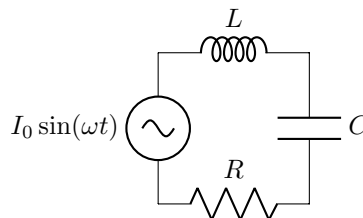

**Exercise 7. Resonance II**

Find the phase angles  $\theta(V_L(t))$ ,  $\theta(V_C(t))$  and  $\theta(V_R(t))$  for the circuit when driven at the resonance frequency.

### Exercise 8. Impedant Circuit I

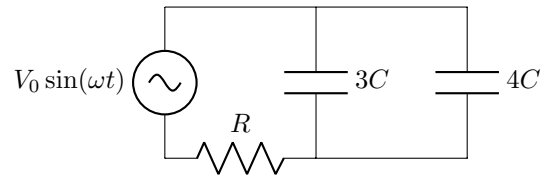

What is the equivalent impedance of the circuit above as measured across the voltage source? What is  $|Z|$ ?

### Exercise 9. Impedant Circuit II


Find  $V_R(t)$  and  $V_{3C}(t)$ . Does  $V_{3C}(t) = V_{4C}(t)$ ?

### Exercise 10. Impedant Circuit III

Find  $\theta(V_R(t))$  and  $\theta(V_{3C}(t))$ , what is the phase difference. Is it constant?

### Exercise 11. Resonance Again


Consider the circuit below:

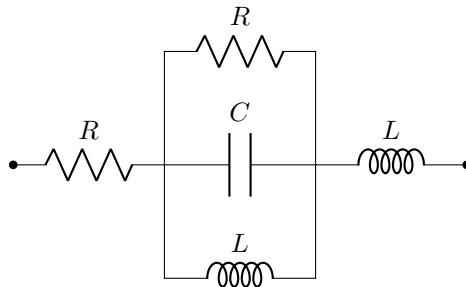

Express the impedance of this circuit in the form  $Z_{\text{circuit}} = a + bi$  for real numbers  $a$  and  $b$ . If  $C = 0$ , what is the resonance frequency of the circuit?


### Exercise 12. Another Circuit

Consider the circuit below:

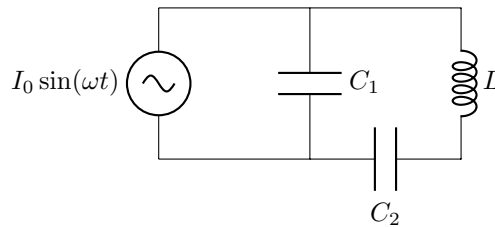

Supposing that  $C_1 = C_2 = C$ , what is  $\theta(V_{C_1}(t))$ ?  $\theta(V_{C_2}(t))$ ?

### Exercise 13. Equivalent Circuits I

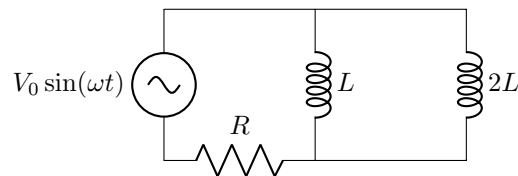

Convert the circuit above into an equivalent circuit with one resistor,  $R'$ , and one inductor,  $L'$ . Explain why the phase angle in this equivalent circuit are the same as the phase angles in the original circuit.

### Exercise 14. Equivalent Circuits II

Using the equivalent circuit from the last problem, find the phase angles  $\theta(V_R) = \theta(V_{R'})$  and  $\theta(V_L) = \theta(V_{L'})$ .