

Analyzing Circuits with Impedances

Ohm's Law:

$$V = IZ \quad (1)$$

Where:¹

$$Z_R = R \quad (2)$$

$$Z_L = i\omega L \quad (3)$$

$$Z_C = 1/i\omega C \quad (4)$$

In series:

$$Z = Z_1 + Z_2 + \dots + Z_n \quad (5)$$

In parallel:


$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \quad (6)$$

Example: Amplitudes when driven by voltage

When we are only interested in voltage and current amplitudes and not phases, we use:

$$Z \mapsto |Z| = \sqrt{[\text{Re}(Z)]^2 + [\text{Im}(Z)]^2} \quad (7)$$

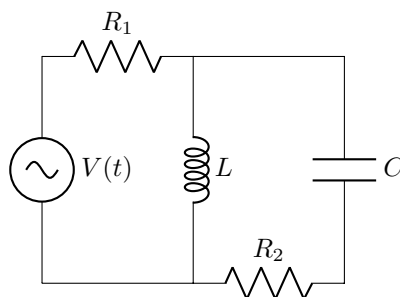Consider the circuit below with $V(t) = V_0 \cos(\omega t)$:



What is the impedance of everything to the right of the battery? Express in the form $Z = R + i\chi$ for real R and χ .

Using series and parallel rules followed by complex arithmetic:²

$$Z = Z_{R_1} + \frac{1}{\frac{1}{Z_L} + \frac{1}{Z_C + Z_{R_2}}} \quad (8)$$

$$= Z_{R_1} + \frac{Z_L(Z_C + Z_{R_2})}{Z_C + Z_{R_2} + Z_L} \quad (9)$$

$$= R_1 + \frac{i\omega L((1/i\omega C) + R_2)}{(1/i\omega C) + R_2 + i\omega L} \quad (10)$$

$$= R_1 + \frac{L/C + i(\omega L R_2)}{R_2 + i(\omega L - 1/\omega C)} \cdot \frac{R_2 - i(\omega L - 1/\omega C)}{R_2 - i(\omega L - 1/\omega C)} \quad (11)$$

$$= R_1 + \frac{[LR_2/C + (\omega L R_2)(\omega L - 1/\omega C)] + i[(\omega L R_2^2) - (L/C)(\omega L - 1/\omega C)]}{R_2^2 + (\omega L - 1/\omega C)^2} \quad (12)$$

$$= \left[R_1 + \frac{LR_2/C + (\omega L R_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] + i \left[\frac{(\omega L R_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \quad (13)$$

¹ $Z = \text{Re}(Z) + i \text{Im}(Z) = R + i\chi$ for resistance R and reactance χ .

² $i^2 = -1$ so $1/i = -i$

What is the maximum current amplitude through R_1 ?

We consider Ohm's law as $V^{\max} = I^{\max}|Z|$, with Z given by (13), with the current at its maximum amplitude when the voltage is at its maximum amplitude $V(t) = V_0$. Then the current through R_1 is the current that goes through the circuit as a whole and it given by:

$$I_{R_1}^{\max} = \frac{V_0}{|Z|} \quad (14)$$

$$= \frac{V_0}{\sqrt{\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2 + \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2}} \quad (15)$$

What is the maximum voltage amplitude through R_2 ?

By charge conservation, we know that the current that flows through the inductor plus the current that flows through R_2 is equal to the current that flows through R_1 , so we have:

$$I_{R_1} = I_L + I_{R_2} \implies I_{R_1}^{\max} = I_L^{\max} + I_{R_2}^{\max} \quad (16)$$

Additionally, since energy is single-valued, the voltage drop across the inductor must equal the voltage drop across the capacitor and R_2 , so:

$$I_L Z_L = I_{R_2} (Z_C + Z_{R_2}) \quad (17)$$

Now, working with magnitudes, $I_{R_1} = I_{R_1}^{\max}$ as in (14-15), and $|Z_L| = \omega L$, and $|Z_C + Z_{R_2}| = \sqrt{R_2^2 + 1/(\omega C)^2}$, so we have two equations and two unknowns, solving we find:

$$I_L^{\max} = \frac{|Z_C + Z_{R_2}|^2}{|Z_L| + |Z_C + Z_{R_2}|} I_{R_1}^{\max} \quad (18)$$

$$I_{R_2}^{\max} = \frac{|Z_L| \cdot |Z_C + Z_{R_2}|}{|Z_L| + |Z_C + Z_{R_2}|} I_{R_1}^{\max} \quad (19)$$

Or, substituting in:

$$I_L^{\max} = \frac{R_2^2 + 1/(\omega C)^2}{\omega L + \sqrt{R_2^2 + 1/(\omega C)^2}} \cdot \frac{V_0}{\sqrt{\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2 + \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2}} \quad (20)$$

$$I_{R_2}^{\max} = \frac{\omega L \sqrt{R_2^2 + 1/(\omega C)^2}}{\omega L + \sqrt{R_2^2 + 1/(\omega C)^2}} \cdot \frac{V_0}{\sqrt{\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2 + \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2}} \quad (21)$$

Thus, the maximum voltage amplitude through R_2 is:

$$V_{R_2}^{\max} = I_{R_2}^{\max} R_2 \quad (22)$$

with $I_{R_2}^{\max}$ as in (21).

What is the phase difference between the voltage in R_1 and R_2 ?

Since both components are resistors, this is equivalent to asking the phase difference between the currents. Now, we cannot use $I_{R_1}^{\max}$ and $I_{R_2}^{\max}$ since these are magnitudes with no phase information.

We have:

$$I_{R_1}(t) = \frac{V_0 \cos(\omega t)}{Z} \quad (23)$$

$$= \frac{V_0 \cos(\omega t)}{\sqrt{\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2 + \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2}} \quad (24)$$

$$\times \left(\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] - i \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \right) \quad (25)$$

In general, the phase is:

$$\theta(f(t)) = \tan^{-1} \left(\frac{\text{Im}(f(t))}{\text{Re}(f(t))} \right) \quad (26)$$

So, we see:

$$\theta_{R_1} = \tan^{-1} \left(-\frac{\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2}}{R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2}} \right) \quad (27)$$

$$= \tan^{-1} \left(-\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_1(R_2^2 + (\omega L - 1/\omega C)^2) + LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)} \right) \quad (28)$$

Now:

$$I_{R_2}(t) = \frac{Z_L(Z_C + Z_{R_2})}{Z_L + Z_C + Z_{R_2}} I_{R_1}(t) \quad (29)$$

$$= \frac{[LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)] + i[\omega LR_2^2 - (L/C)(\omega L - 1/\omega C)]}{R_2^2 + (\omega L - 1/\omega C)^2} I_{R_1}(t) \quad (30)$$

$$= \frac{[LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)] + i[\omega LR_2^2 - (L/C)(\omega L - 1/\omega C)]}{1} \quad (31)$$

$$\times \frac{1}{R_2^2 + (\omega L - 1/\omega C)^2} \frac{V_0 \cos(\omega t)}{\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2 + \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2} \quad (32)$$

$$\times \left(\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] - i \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \right) \quad (33)$$

$$= \frac{1}{R_2^2 + (\omega L - 1/\omega C)^2} \frac{V_0 \cos(\omega t)}{\left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2 + \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]^2} \quad (34)$$

$$\times \left\{ \left([LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)] \left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \right) \right. \quad (35)$$

$$\left. + [\omega LR_2^2 - (L/C)(\omega L - 1/\omega C)] \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \right) \quad (36)$$

$$+ i \left([\omega LR_2^2 - (L/C)(\omega L - 1/\omega C)] \left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \right) \quad (37)$$

$$\left. - [LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)] \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] \right) \left. \right\} \quad (38)$$

So:

$$\theta_{R_2} = \tan^{-1} \left(\frac{[\omega LR_2^2 - (L/C)(\omega L - 1/\omega C)] \left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] - [LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)] \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]}{[LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)] \left[R_1 + \frac{LR_2/C + (\omega LR_2)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right] + [\omega LR_2^2 - (L/C)(\omega L - 1/\omega C)] \left[\frac{(\omega LR_2^2) - (L/C)(\omega L - 1/\omega C)}{R_2^2 + (\omega L - 1/\omega C)^2} \right]} \right) \quad (39)$$

If we have a 1 kHz signal with both resistors of 10 Ω , a capacitor of 1000 μF , and a 1 mH inductor, then:

$$\theta_{R_1} = -19.37^\circ \quad (40)$$

$$\theta_{R_2} = 38.24^\circ \quad (41)$$

where V_{R_1} lags the voltage by 19.37°, and V_{R_2} leads the voltage by 38.24°, for a phase difference of:

$$|\theta_{R_1} - \theta_{R_2}| = 57.61^\circ \quad (42)$$